

CPE 233 HW 5

Wyatt Tack


1. Behavior Description: The Branch address generator and condition generators are used to manipulate the program counter based on the different jump and branch commands available in the RISC-V assembler code. The address generator creates the new program count address based on the combination of the different immediates along with the current program count, or in case of the JALR command the register data inputted. The condition generator evaluates the two compared registers for the branch commands that would branch if the condition is met, as the condition generator gives a 1 for true and a 0 for false for the 3 needed commands: equal, less than, and less than unsigned.

Lastly is the Memory module, which contains the stored and data that the registers read and write to, containing more referenceable memory, access to MMIO, the stack, and stores the program machine code referenced in the first address. The second address uses asynchronous read and write to manipulate the data segment, stack, and MMIO (MMIO through IO_WR and IO_IN).


Signal Name	Size (Bits)	Purpose
MEM_CLK	1	Clock signal for synchronous actions, data stored so clock is needed
MEM_RDEN1	1	Read enable for Address 1, aka the program counter
MEM_RDEN2	1	Read enable for Address 2, being the memory that the program executed will read from
MEM_WE2	1	Write enable for Address 2, being the only access to alter the data stored in address 2 (Data/Stack/ MMIO)
MEM_ADDR1	14	Address of data to output in MEM_DOUT1, connected to the program counter as input to program memory
MEM_ADDR2	32	Address for all other data to access to either read or write from (Data/Stack/ MMIO)
MEM_DIN2	32	Data inputted to be written over address 2 data (Data/Stack/ MMIO) from write instructions
MEM_SIZE	2	Determines the size of the data to be loaded out of MEM_DOUT2, whether it be a word, byte, or half word
MEM_SIGN	1	Determines if smaller data sizes (byte/ halfword) are to be sign extended when being read to the 32-bit value MEM_DOUT2
IO_IN	32	Data stream to/from MMIO, i.e. switches and LEDs on basys board
IO_WR	1	Read/write determining bit for MMIO data, i.e. read from switches, write to LEDs
MEM_DOUT1	32	Outputs data stored at address 1, used to output machine code determined by program counter and program memory
MEM_DOUT2	32	Outputs data stored at address 2 to reg_file (Data/Stack/ MMIO)

2. Structural Design:

Branch Condition Generator:

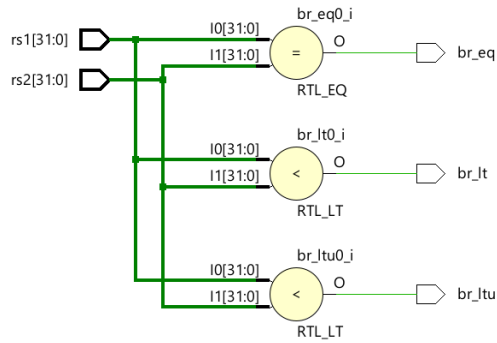


Branch Address Generator:

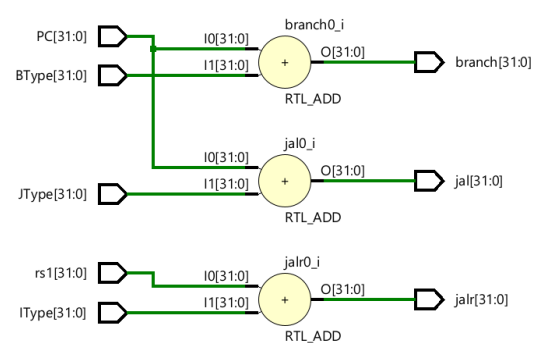


3. Synthesis Warnings Listing:

a. Branch Condition Generator:

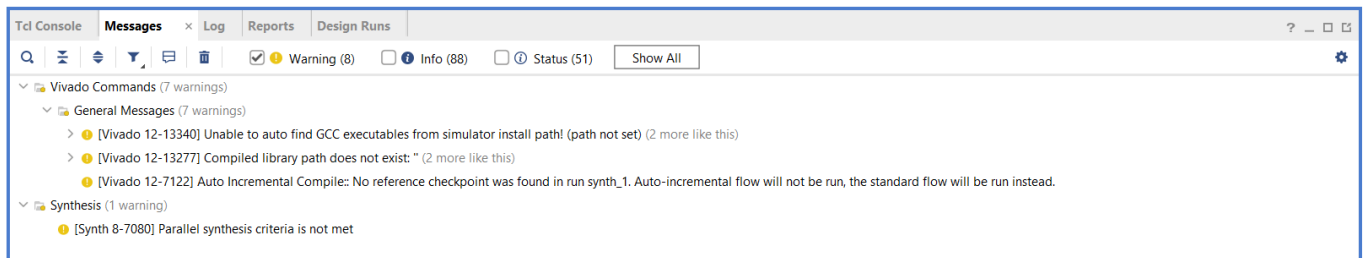

b. Branch Address Generator

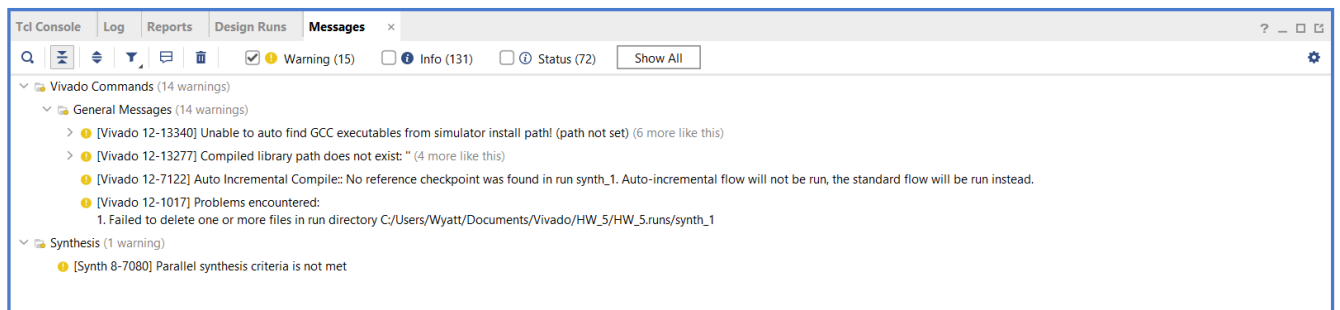

4. Verification:

a. Table for Branch Condition Generator:

Test Case Input	Test Case Output	Test Case Reasoning
rs1 = 0x00001000 rs2 = 0x10000000	eq = 0 lt = 1 ltu = 1	Tests lt and ltu
rs1 = 0x 00000100 rs2 = 0x 00000010	eq = 0 lt = 0 ltu = 0	Tests no conditions met
rs1 = 0x 02050a00 rs2 = 0x 02050a00	eq = 1 lt = 0 ltu = 0	Tests equal only
rs1 = 0x 00001000 rs2 = 0x 80010000	eq = 0 lt = 0 ltu = 1	Tests ltu only
rs1 = 0x00000000 rs2 = 0x00000000	eq = 1 lt = 0 ltu = 0	Tests eq again at 0
rs1 = 0x 40000000 rs2 = 0x 00000000	eq = 0 lt = 0 ltu = 0	Tests no conditions met
rs1 = 0x 00000000 rs2 = 0x04000000	eq = 0 lt = 1 ltu = 1	Tests lt and ltu at 0
rs1 = 0x00000000 rs2 = 0xffffffff	eq = 0 lt = 0 ltu = 1	Tests just ltu at edge
rs1 = 0xffffffff rs2 = 0x00000000	eq = 0 lt = 1 ltu = 0	Tests just lt at edge

b. Table for Branch Address Generator

Test Case Input	Test Case Output	Test Case Reasoning
PC = 0x ffff0000 rs1 = 0x d2d2000 JType = 0x 0000a1a1 BType = 0x 0000b2b2 IType = 0x 0000c3c3	jal = 0xffffa1a1 branch = 0xffffb2b2 jalr = 0x0d2dec3	Tests standard operation
PC = 0x a1a11111 rs1 = 0x b2b22222 JType = 0x 01011111 BType = 0x 02022222 IType = 0x 03033333	jal = 0xa2a22222 branch = 0xa3a33333 jalr = 0xb5b55555	Tests standard addition again
PC = 0x ffffffff rs1 = 0x afffffff2 JType = 0x 00000004 BType = 0x 00000003 IType = 0x 80000000	jal = 0x00000000 branch = 0xffffffff jalr = 0x2fffffff2	Tests overflow and edge cases

Simulation:

- Branch Condition Generator:

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns	40.000 ns	50.000 ns	60.000 ns	70.000 ns	80.000 ns	90.000 ns	100.000 ns
> rs1[31:0]	00001000	xxxxxxxx	00001000	00000100	02050a00	00001000	00000000	40000000	00000000	00000000	fffffffe	
> rs2[31:0]	10000000	xxxxxxxx	10000000	00000010	02050a00	80010000	00000000	04000000	fffffffe	00000000		
br_eq	0											
br_lt	1											
br_ltu	1											

- Branch Address Generator:

Name	Value	0.000 ns	5.000 ns	10.000 ns	15.000 ns	20.000 ns	25.000 ns	30.000 ns	35.000 ns	40.000 ns
> PC[31:0]	ffff0000	xxxxxxxx		ffff0000		a1a11111		fffffffc		
> rs1[31:0]	0d2d2000	xxxxxxxx		0d2d2000		b2b22222		ffffffe2		
> JType[31:0]	0000a1a1	xxxxxxxx		0000a1a1		01011111		00000004		
> BType[31:0]	0000b2b2	xxxxxxxx		0000b2b2		02022222		00000003		
> IType[31:0]	0000c3c3	xxxxxxxx		0000c3c3		03033333		80000000		
> jal[31:0]	ffffa1a1	xxxxxxxx		ffffa1a1		a2a22222		00000000		
> branch[31:0]	ffffb2b2	xxxxxxxx		ffffb2b2		a3a33333		fffffffe		
> jalr[31:0]	0d2de3c3	xxxxxxxx		0d2de3c3		b5b55555		2ffffffe		

5. System Verilog Source Code:

For Branch Condition Generator:

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: Cal Poly SLO
// Engineer: Wyatt Tack
//
// Create Date: 02/01/2024
// Design Name: Branch Condition Generator
// Project Name: OTTER MCU
// Target Devices: Basys 3 Board
// Description: Generates the 3 conditions between rs1 and rs2
//              being =, <, and < Signed on OTTER MCU
//
/////////////////////////////////////////////////////////////////
module Branch_Cond_Gen(
    input [31:0] rs1, rs2,
    output logic br_eq, br_lt, br_ltu
);
    always_comb //combinational block, set conditionals to binary
    begin //true/false based on evaluation:
        br_eq = (rs1 == rs2);
        br_lt = ($signed(rs1) < $signed(rs2));
        br_ltu = (rs1 < rs2);
    end
endmodule

```

For Branch Condition Generator Simulation Test Bench:

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: Cal Poly SLO
// Engineer: Wyatt Tack
//
// Create Date: 02/01/2024
// Design Name: Branch Condition Generator Simulation
// Project Name: OTTER MCU
// Target Devices: Basys 3 Board
// Description: Generates the 3 conditions between rs1 and rs2
//              being =, <, and < Signed on OTTER MCU
//              Simulation Source
/////////////////////////////////////////////////////////////////
module Branch_Cond_Gen_TB();
logic [31:0] rs1, rs2;
logic br_eq, br_lt, br_ltu;
Branch_Cond_Gen UUT
(.rs1(rs1), .rs2(rs2), .br_eq(br_eq), .br_lt(br_lt), .br_ltu(br_ltu));
always begin
#10 rs1 = 32'h00001000; //lt, ltu
    rs2 = 32'h10000000;
#10 rs1 = 32'h00000100; //none
    rs2 = 32'h00000010;
#10 rs1 = 32'h02050a00; //eq
    rs2 = 32'h02050a00;
#10 rs1 = 32'h00001000; //ltu
    rs2 = 32'h80010000;
#10 rs1 = 32'h00000000; //eq
    rs2 = 32'h00000000;
#10 rs1 = 32'h40000000; //none
    rs2 = 32'h00000000;
#10 rs1 = 32'h00000000; //lt, ltu
    rs2 = 32'h04000000;
#10 rs1 = 32'h00000000; //ltu
    rs2 = 32'hfffffff;
#10 rs1 = 32'hfffffff; //lt
    rs2 = 32'h00000000;
end
endmodule
```

For Branch Address Generator:

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: Cal Poly SLO
// Engineer: Wyatt Tack
//
// Create Date: 02/01/2024
// Design Name: Branch Address Generator
// Project Name: OTTER MCU
// Target Devices: Basys 3 Board
// Description: Generates the jumped to address based on the
//              current PC and immediates for Jump types,
//              and RS2
/////////////////////////////////////////////////////////////////
module Branch_Add_Gen(
input [31:0] PC, JType, BType, IType, rs1,
output logic [31:0] jal, branch, jalr
);
always_comb
begin
    jal = PC + JType;           //set next program address as what
    branch = PC + BType;       //each instruction is defined as
    jalr = rs1 + IType;        //in assembler manual
end
endmodule
```

For Branch Address Generator Simulation Test Bench:

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: Cal Poly SLO
// Engineer: Wyatt Tack
//
// Create Date: 02/01/2024
// Design Name: Branch Address Generator Test Bench
// Project Name: OTTER MCU
// Target Devices: Basys 3 Board
// Description: Generates the jumped to adress based on the
//              current PC and immediates for Jump types,
//              and RS2 Simulation Source
/////////////////////////////////////////////////////////////////

module Branch_Add_Gen_TB();
logic [31:0] PC, JType, BType, IType, rs1;
logic [31:0] jal, branch, jalr;

Branch_Add_Gen UUT (.PC(PC), .JType(JType), .BType(BType),
                    .IType(IType), .rs1(rs1), .jal(jal),
                    .branch(branch), .jalr(jalr));

always
begin
#10 PC = 32'hffff0000;
    rs1 = 32'h0d2d2000;
    JType = 32'h0000a1a1; //jal = +PC
    BType = 32'h0000b2b2; //branch = +PC
    IType = 32'h0000c3c3; //jalr = +rs1
#10 PC = 32'ha1a11111;
    rs1 = 32'hb2b22222;
    JType = 32'h01011111; //jal = +PC
    BType = 32'h02022222; //branch = +PC
    IType = 32'h03033333; //jalr = +rs1
#10 PC = 32'hffffffc;
    rs1 = 32'haffffff2;
    JType = 32'h00000004; //jal = +PC
    BType = 32'h00000003; //branch = +PC
    IType = 32'h80000000; //jalr = +rs1
end
endmodule
```