 



CPE 233 HW 7

Wyatt Tack

1. Behavior Description: The OTTER Wrapper functions as the device that connects the OTTER MCU to the various In and Out that wished to be read or written to for the program to work. For example, it's the wrapper's job to funnel in all the drivers to and from external inputs (such as the switches on the basys 3 board) to the IOBUS_IN input on the MCU, to be read as memory. The same applies for the outputs, in which if data is wished to be written to the 7 segment display on the board, then the wrapper is responsible for connecting the IOBUS_OUT to the specific seven segment display driver and leds, along with the address select and write enable.
2. Structural Design for whole OTTER:



- ### 3. Synthesis Warnings Listing:

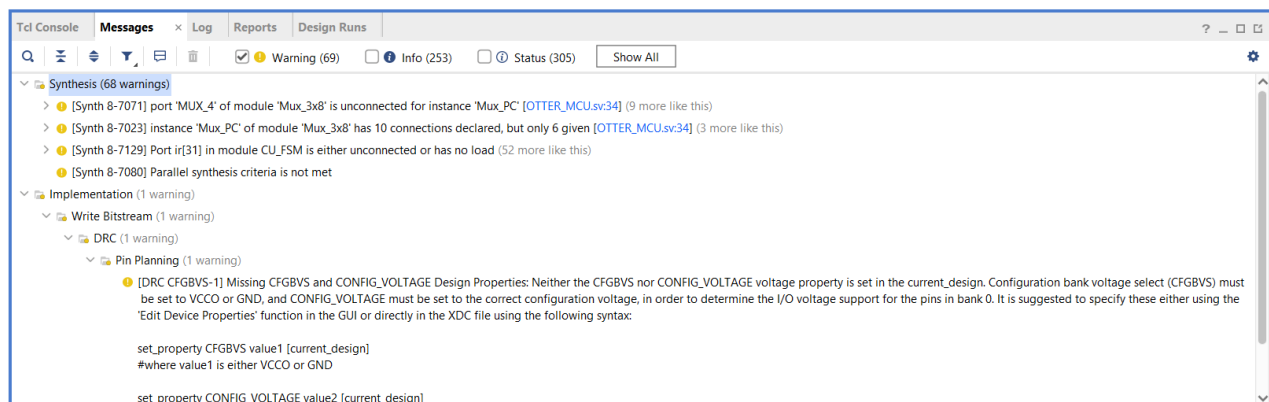

- #### 4. Verification:

Test File uploaded to board and to be shown to Professor in class

5. System Verilog Source Code:

For Control Unit Decoder:

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: Cal Poly SLO
// Engineer: Wyatt Tack
//
// Create Date: 02/01/2024
// Design Name: Control Unit Decoder
// Project Name: OTTER MCU
// Target Devices: Basys 3 Board
// Description: Sends non timing dependent selection signals
//              for data manipulation in otter MCU
//
/////////////////////////////////////////////////////////////////

module CU_DECODER(
input [31:0] ir,
input br_eq, br_lt, br_ltu,
//input int_taken
output logic [2:0] ALU_FUN,
output logic [1:0] srcA_SEL,
output logic [2:0] srcB_SEL,
output logic [2:0] PC_SEL,
output logic [2:0] RF_SEL,
output logic [1:0] RF_SEL
);
always comb begin
    ALU_FUN = 0;
    srcA_SEL = 0;
    srcB_SEL = 0;
    PC_SEL = 0;
    RF_SEL = 0;
    case (ir[6:0]) //op-codes
        7'b0110011: //All R-Type
            begin
                ALU_FUN = {ir[30], ir[14:12]};
                srcA_SEL = 0;
                srcB_SEL = 0;
                PC_SEL = 0;
                RF_SEL = 3;
            end
        7'b0010011: //1st set of I-Type Instructions
            begin
                if (ir[14:12] == 3'b101) ALU_FUN = {ir[30], ir[14:12]};
                else ALU_FUN = {1'b0, ir[14:12]};
                srcA_SEL = 0;
                srcB_SEL = 1;
                PC_SEL = 0;
                RF_SEL = 3;
            end
        7'b0000011: //2nd set of I-Type Instructions
            begin
                ALU_FUN = 4'b0000;
                srcA_SEL = 0;
                srcB_SEL = 1;
                PC_SEL = 0;
                RF_SEL = 2;
            end
        7'b1100111: //Last set of I-Type (for jalr)
            begin
                PC_SEL = 1;
                RF_SEL = 0;
            end
        7'b0100011: //All S-Type Instructions
            begin
                ALU_FUN = 4'b0000;
                srcA_SEL = 0;
                srcB_SEL = 2;
                PC_SEL = 0;
            end
        7'b1100011: //All B-Type Instructions (include conditions)
            begin
                case(ir[14:13])
                    2'b00: //equal
                        begin
                            PC_SEL = {1'b0, (ir[12]^br_eq),1'b0};
                        end
                    2'b01: //less than
                        begin
                            PC_SEL = {1'b0, (ir[12]^br_lt),1'b0};
                        end
                    2'b11: //less than unsigned
                        begin
                            PC_SEL = {1'b0, (ir[12]^br_ltu),1'b0};
                        end
                    default:
                        begin
                            PC_SEL = 0;
                        end
                endcase
            end
        7'b0110111: //1st set of U-Type (lui)
            begin
                ALU_FUN = 4'b1001;
                srcA_SEL = 1;
                PC_SEL = 0;
                RF_SEL = 3;
            end
        7'b0010111: //2nd set of U-Type (auipc)
            begin
                //auipc*****auipc
                ALU_FUN = 4'b0000;
                srcA_SEL = 1;
                srcB_SEL = 3;
                PC_SEL = 0;
                RF_SEL = 3;
            end
        7'b1101111: //All J-Type instructions (jal)
            begin
                PC_SEL = 3;
                RF_SEL = 0;
            end
        default:
            begin
                ALU_FUN = 0;
                srcA_SEL = 0;
                srcB_SEL = 0;
                PC_SEL = 0;
                RF_SEL = 0;
            end
        endcase
    end
endmodule
```

For Control Unit FSM:

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: Cal Poly SLO
// Engineer: Wyatt Tack
//
// Create Date: 02/01/2024
// Design Name: Control Unit FSM
// Project Name: OTTER MCU
// Target Devices: Basys 3 Board
// Description: Sends selection signals for timing specific
//               operations in memory of OTTER MCU
//
/////////////////////////////////////////////////////////////////

module CU_FSM(
input RST, clk,
//input INTR,
input [31:0] ir,
output logic PC_WE, RF_WE, memWE2, memRDEN1, memRDEN2, reset
//output logic csr_WE, int_taken, mret_exec
);

typedef enum {ST_INIT, ST_FETCH, ST_EXEC, ST_WRITE} state_type;
state_type NS, PS;
always_ff@(posedge clk) begin //state register
    if(RST == 1) PS<=ST_INIT;
    else PS<=NS;
end

always_comb begin //input/output logic
    PC_WE = 0;
    RF_WE = 0;
    memWE2 = 0;
    memRDEN1 = 0;
    memRDEN2 = 0;
    reset = 0;
    // csr_WE = 0;
    // int_taken = 0;
    // mret_exec = 0;
    case(PS)
        ST_INIT: begin
            reset = 1'b1;
            NS = ST_FETCH;
        end
        ST_FETCH: begin
            memRDEN1 = 1'b1;
            NS = ST_EXEC;
        end
        ST_EXEC: begin
            NS = ST_FETCH;
            case (ir[6:0]) //op-codes
                7'b0110011: //All R-Type
                    begin
                        PC_WE = 1;
                        RF_WE = 1;
                    end
                7'b0010011: //1st set of I-Type Instructions
                    begin
                        PC_WE = 1;
                        RF_WE = 1;
                    end
                7'b0000011: //2nd set of I-Type Instructions
                    begin
                        NS = ST_WRITE;
                        memRDEN2 = 1;
                    end
                7'b1100111: //Last set of I-Type (for jalr)
                    begin
                        PC_WE = 1;
                        RF_WE = 1;
                    end
                7'b0100011: //All S-Type Instructions
                    begin
                        PC_WE = 1;
                        memWE2 = 1;
                    end
                7'b1100011: //All B-Type Instructions (include conditions)
                    begin
                        PC_WE = 1;
                    end
                7'b0110111: //1st set of U-Type (lui)
                    begin
                        PC_WE = 1;
                        RF_WE = 1;
                    end
                7'b0010111: //2nd set of U-Type (auipc)
                    begin
                        PC_WE = 1;
                        RF_WE = 1;
                    end
                7'b1101111: //All J-Type instructions (jal)
                    begin
                        PC_WE = 1;
                        RF_WE = 1;
                    end
                default:
                    begin
                    end
            endcase
        end
        ST_WRITE: begin
            NS = ST_FETCH;
            PC_WE = 1;
            RF_WE = 1;
        end
        default: begin
            NS = ST_INIT;
        end
    endcase
end
endmodule
```