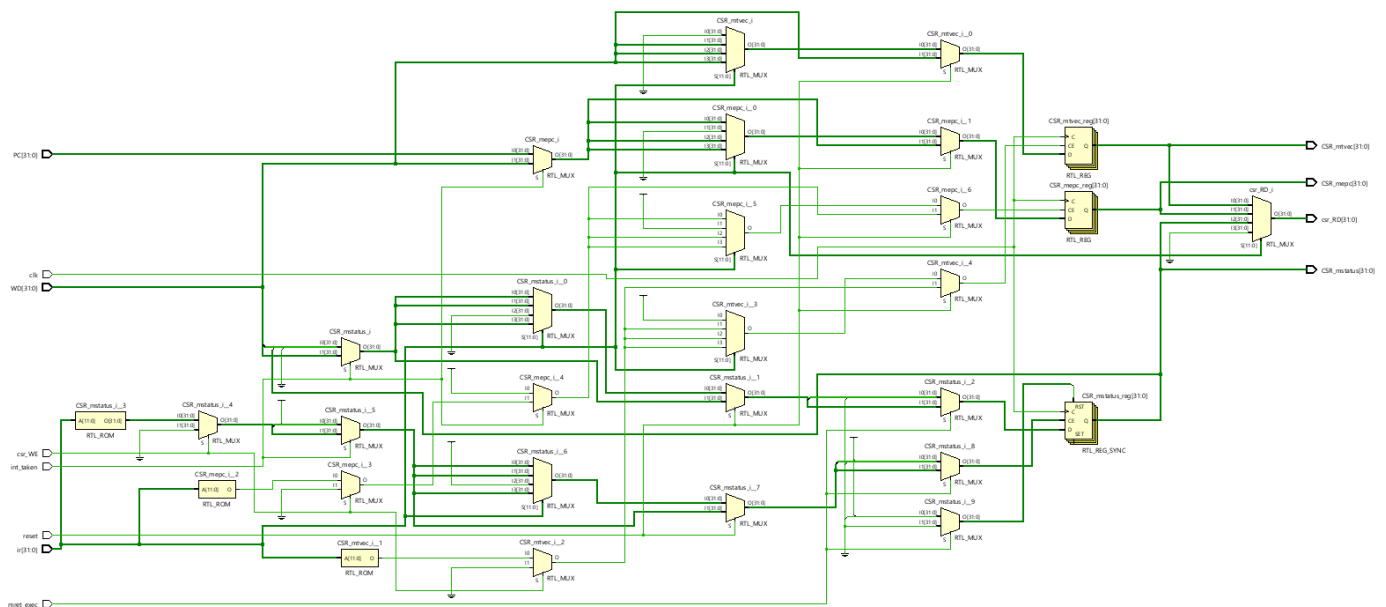


# CPE 233 HW 8


Wyatt Tack

1. **Behavior Description:** The CSR functions as a separate register file, relating specifically to the interrupt service routine. Three main registers are stored in the CSR, being the program address for the service routing (MTVEC), the interrupt enable status (MTSTATUS), and the stored current program count when an interrupt is pressed (MEPC). These addresses can be written to and read from, and are output asynchronously to the control unit FSM to determine what to do when an interrupt signal occurs.

- ## 2. Structural Design for CSR:




- ### 3. Synthesis Warnings Listing:

 


4. Verification (specified instructions executed after time marker):


CSRRW:

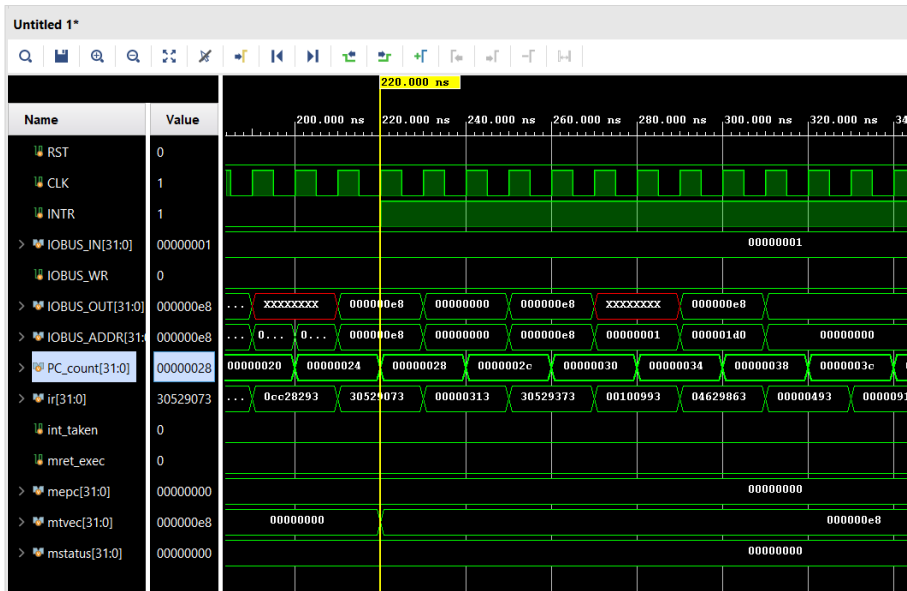


CSRRS:

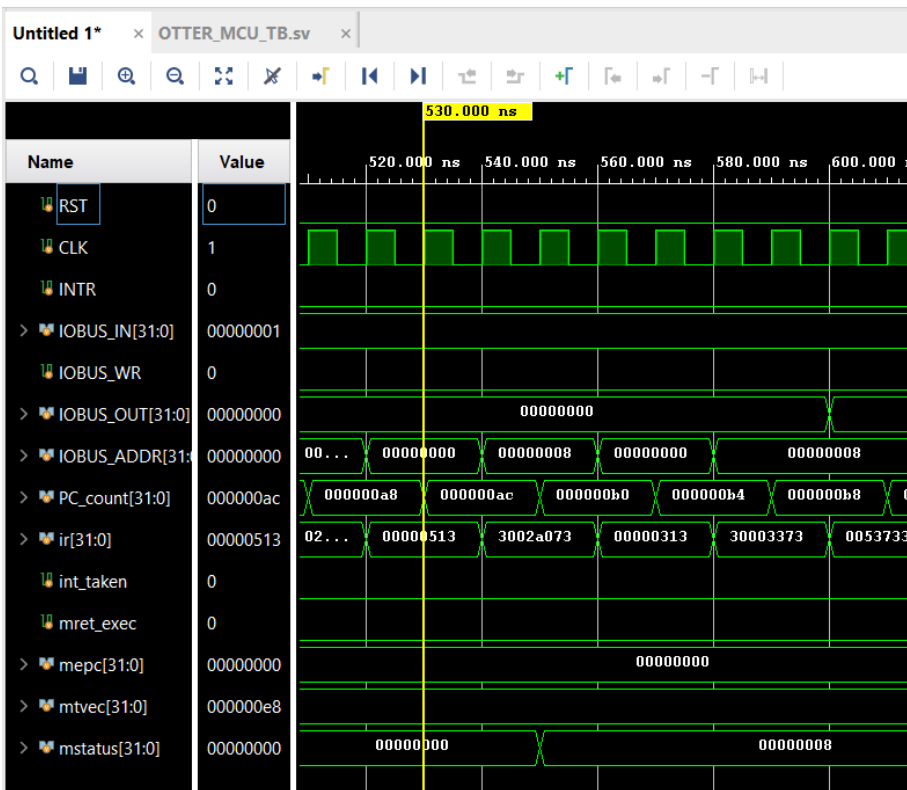

CSRRC:

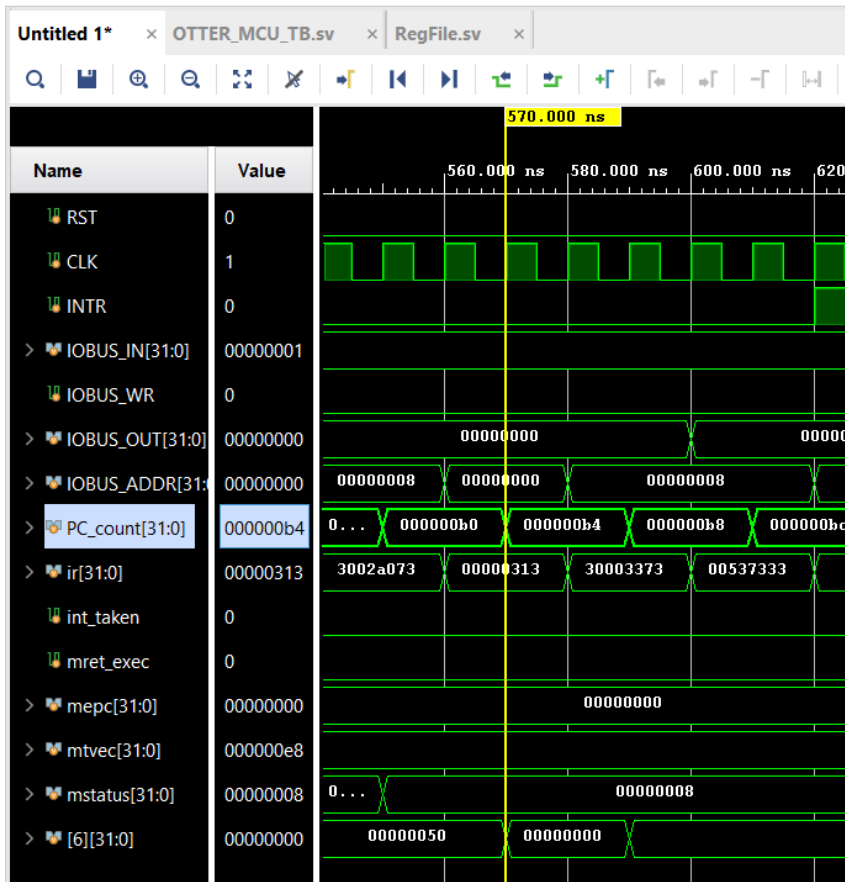

INTR:

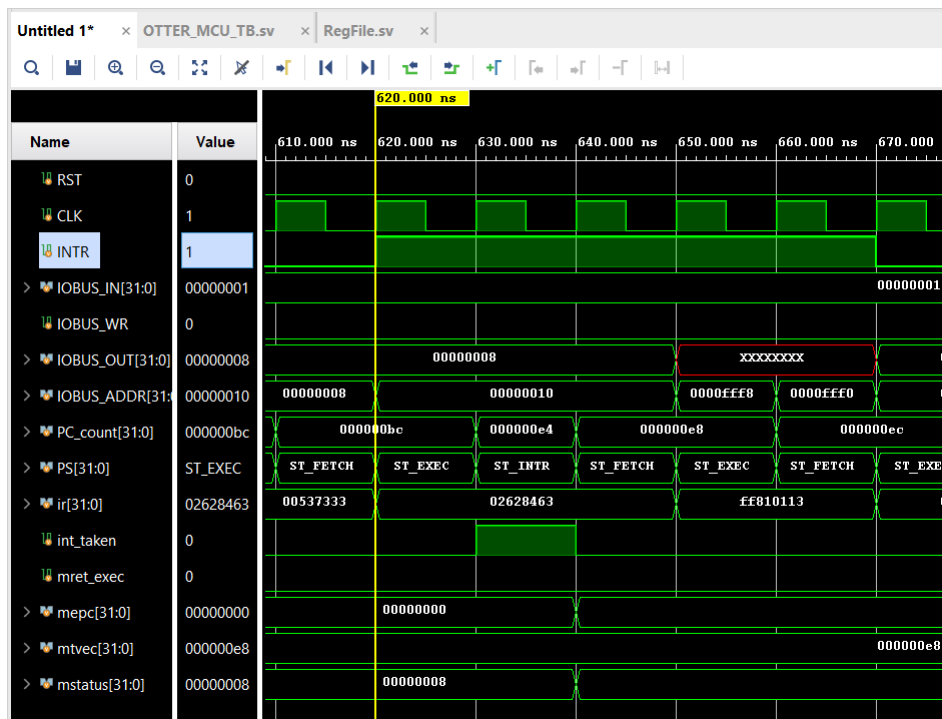

## MRET:



## 5. System Verilog Source Code:

### For Control System Registers:

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: Cal Poly SLO
// Engineer: Wyatt Tack
//
// Create Date: 02/29/2024
// Design Name: Control Status Registers
// Project Name: OTTER MCU
// Target Devices: Basys 3 Board
// Description: Registers that hold data for interrupts
//
/////////////////////////////////////////////////////////////////
module CSR(
input clk,
input reset, mret_exec, int_taken, csr_WE,
input [31:0] ir, PC, WD,
output logic[31:0] CSR_mstatus, CSR_mepc, CSR_mtvec,
output logic[31:0] csr_RD
);
always_ff@(posedge clk)
begin
    if(csr_WE == 1) //write data synchronously
    begin
        case(ir[31:20])
            12'h305: CSR_mtvec <= WD;
            12'h341: CSR_mepc <= WD;
            12'h300: CSR_mstatus <= WD;
        endcase
    end
    if(int_taken == 1) //when interrupt
    begin
        CSR_mepc <= PC;
        CSR_mstatus[7] <= CSR_mstatus[3];
        CSR_mstatus[3] <= 1'b0;
    end
    if(reset == 1) //if reset
    begin
        CSR_mtvec <= 0;
        CSR_mepc <= 0;
        CSR_mstatus <= 0;
    end
    if(mret_exec == 1) //when intr end, reset status enable
    begin
        CSR_mstatus[3] <= CSR_mstatus[7];
        CSR_mstatus[7] <= 1'b0;
    end
end
always_comb begin
    case(ir[31:20]) //output asynch read
        12'h305: csr_RD = CSR_mtvec;
        12'h341: csr_RD = CSR_mepc;
        12'h300: csr_RD = CSR_mstatus;
        default: csr_RD = 0;
    endcase
end
endmodule

```

## For Control Unit Decoder:

```
timescale 1ns / 1ps
// Company: Cal Poly SLO
// Engineer: Wyatt Tack
//
// Create Date: 02/01/2024
// Design Name: Control Unit Decoder
// Project Name: OTTER MCU
// Target Devices: Easys 3 Board
// Description: Sends non timing dependent selection signals
//              for data manipulation in otter MCU
//
//
//
module CU_CDR(
    input [31:0] ir,
    input br_eq, br_lt, br_ltu,
    input int_taken,
    output logic [3:0] ALU_FUN,
    output logic [1:0] srcA_SEL,
    output logic [2:0] srcB_SEL,
    output logic [2:0] PC_SEL,
    output logic [1:0] RF_SEL
);
always_comb begin
    ALU_FUN = 0;
    srcA_SEL = 0;
    srcB_SEL = 0;
    PC_SEL = 0;
    RF_SEL = 0;
    case (ir[6:0]) //op-codes
        7'b0110011: //All R-Type
            begin
                ALU_FUN = {ir[30], ir[14:12]};
                srcA_SEL = 0;
                srcB_SEL = 0;
                PC_SEL = 0;
                RF_SEL = 3;
            end
        7'b0010011: //1st set of I-Type Instructions
            begin
                if (ir[14:12] == 3'b101) ALU_FUN = {ir[30], ir[14:12]};
                else ALU_FUN = {1'b0, ir[14:12]};
                srcA_SEL = 0;
                srcB_SEL = 1;
                PC_SEL = 0;
                RF_SEL = 3;
            end
        7'b0000011: //2nd set of I-Type Instructions
            begin
                ALU_FUN = 4'b0000;
                srcA_SEL = 0;
                srcB_SEL = 1;
                PC_SEL = 0;
                RF_SEL = 2;
            end
        7'b1100111: //Last set of I-Type (for jalr)
            begin
                PC_SEL = 1;
                RF_SEL = 0;
            end
        7'b0100011: //All S-Type Instructions
            begin
                ALU_FUN = 4'b0000;
                srcA_SEL = 0;
                srcB_SEL = 2;
                PC_SEL = 0;
            end
        7'b1100011: //All B-Type Instructions (include conditions)
            begin
                case(ir[14:13])
                    2'b00: //equal
                        begin
                            PC_SEL = {1'b0, (ir[12]^br_eq),1'b0};
                        end
                    2'b10: //less than
                        begin
                            PC_SEL = {1'b0, (ir[12]^br_lt),1'b0};
                        end
                    2'b11: //less than unsigned
                        begin
                            PC_SEL = {1'b0, (ir[12]^br_ltu),1'b0};
                        end
                    default:
                        begin
                            PC_SEL = 0;
                        end
                endcase
            end
        7'b0110111: //1st set of U-Type (lui)
            begin
                ALU_FUN = 4'b1001;
                srcA_SEL = 1;
                PC_SEL = 0;
                RF_SEL = 3;
            end
        7'b0010111: //2nd set of U-Type (auipc)
            begin
                ALU_FUN = 4'b0000;
                srcA_SEL = 1;
                srcB_SEL = 3;
                PC_SEL = 0;
                RF_SEL = 3;
            end
        7'b1101111: //All J-Type Instructions (jal)
            begin
                PC_SEL = 3;
                RF_SEL = 0;
            end
        7'b1110011: //All CSR instructions
            begin
                if (ir[14:12] == 3'b000) PC_SEL = 5; //if mret, branch to mepc

                else begin
                    RF_SEL = 2'b01;
                    srcB_SEL = 3'b100;
                    case(ir[14:12])
                        3'b011: //c
                            begin
                                ALU_FUN = 4'b0111;
                                srcA_SEL = 2'b10;
                            end
                        3'b010: //s
                            begin
                                ALU_FUN = 4'b0110;
                                srcA_SEL = 2'b00;
                            end
                        3'b001: //w
                            begin
                                ALU_FUN = 4'b1001;
                                srcA_SEL = 2'b00;
                            end
                    endcase
                end
            end
        if (int_taken == 1) PC_SEL = 3'b100; //if interrupt branch to ISR
    endcase
end
endmodule
```

For Control Unit FSM:

```

timescale 1ns / 1ps
// Company: Cal Poly SLO
// Engineer: Wyatt Tack
//
// Create Date: 02/01/2024
// Design Name: Control Unit FSM
// Project Name: OTTER MCU
// Target Devices: Baaya 3 Board
// Description: Sends selection signals for timing specific
//               operations in memory of OTTER MCU
//
// =====//=====

module CU_FSM(
input RST, clk,
input INTR,
input [31:0] Ir,
output logic PC_WE, RF_WE, memWE2, memRDEN1, memRDEN2, reset,
output logic csr_WE, int_taken, mret_exec
);
typedef enum (ST_INIT, ST_FETCH, ST_EXEC, ST_WRITE, ST_INTR) state type;
state type NS, PS;
always_ff@(posedge clk) begin //state register
    if(RST == 1) PS<=ST_INIT;
    else PS<=NS;
end

always_comb begin //input/output logic
    PC_WE = 0;
    RF_WE = 0;
    memWE2 = 0;
    memRDEN1 = 0;
    memRDEN2 = 0;
    reset = 0;
    csr_WE = 0;
    int_taken = 0;
    mret_exec = 0;
case(PS)
    ST_INIT: begin
        reset = 1'b1;
        NS = ST_FETCH;
    end
    ST_FETCH: begin
        memRDEN1 = 1'b1;
        NS = ST_EXEC;
    end
    ST_EXEC: begin
        case (Ir[6:0]) //op-codes
            7'b0110011: //All R-Type
                begin
                    PC_WE = 1;
                    RF_WE = 1;
                end
            7'b0010011: //1st set of I-Type Instructions
                begin
                    PC_WE = 1;
                    RF_WE = 1;
                end
            7'b0000011: //2nd set of I-Type Instructions
                begin
                    memRDEN2 = 1;
                end
            7'b1101111: //Last set of I-Type (for jalr)
                begin
                    PC_WE = 1;
                    RF_WE = 1;
                end
            7'b0100011: //All S-Type Instructions
                begin
                    PC_WE = 1;
                    memWE2 = 1;
                end
            7'b1100011: //All B-Type Instructions (include conditions)
                begin
                    PC_WE = 1;
                end
            7'b0110111: //1st set of U-Type (lui)
                begin
                    PC_WE = 1;
                    RF_WE = 1;
                end
            7'b0010111: //2nd set of U-Type (auipc)
                begin
                    PC_WE = 1;
                    RF_WE = 1;
                end
            7'b1101111: //All J-Type instructions (jal)
                begin
                    PC_WE = 1;
                    RF_WE = 1;
                end
            7'b1110011: //All CSR Instructions
                begin
                    PC_WE = 1;
                    if(Ir[14:12] == 3'b000)mret_exec = 1'b1;
                    else begin
                        csr_WE = 1;
                        RF_WE = 1;
                    end
                end
            endcase
        //state selector
        if (INTR == 1 && Ir[6:0] != 7'b0000011) NS = ST_INTR; //load=INTR->INTR
        else if (Ir[6:0] == 7'b0000011) NS = ST_WRITE; //load=WRITEBACK
        else NS = ST_FETCH; //load=!INTR->FETCH
    end
    ST_WRITE: begin
        //state calculator
        if (INTR == 1) NS = ST_INTR;
        else NS = ST_FETCH;
        PC_WE = 1;
        RF_WE = 1;
    end
    ST_INTR: begin
        int_taken = 1;
        PC_WE = 1;
        NS = ST_FETCH;
    end
    default: begin
        NS = ST_INIT;
    end
endcase
end
endmodule

```