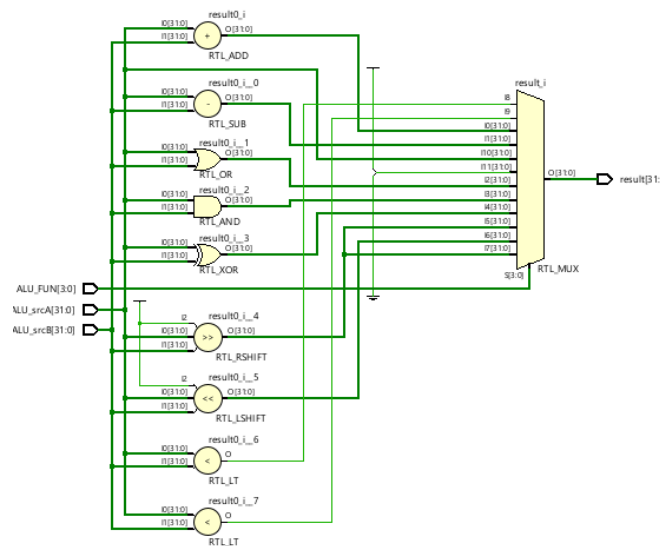


CPE 233 HW 4


Wyatt Tack

1. Behavior Description: The ALU (short for arithmetic logic unit) is the actual operator of the OTTER MCU, in which it performs each of the mathematical, logical, and manipulations to the data stored in the REG_FILE. The design is a combinational circuit that runs each of the 11 operations in parallel and uses a large multiplexor to select which one is to be outputted as the answer. So, all operations possible are performed on the 2 inputs, but the function selector determines which one is actually outputted.

2. Structural Design:



3. Synthesis Warnings Listing:

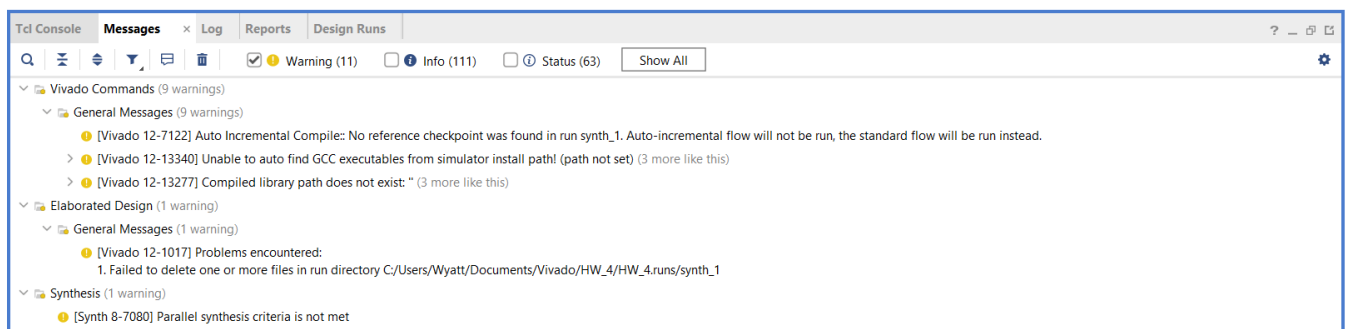

4. Verification:
- a. Table:

Function	ALU_FUN	Arguments		Expected Result (hex)
		A	B	
ADD	0000	0xA50F96C3	0x5AF0693C	FFFFFFFF
	0000	0x84105F21	0x7B105FDE	FF20BEFF
	0000	0xFFFFFFFF	0x00000001	00000000
SUB	1000	0x00000000	0x00000001	FFFFFFFF
	1000	0xAA806355	0x550162AA	557F00AB
	1000	0x550162AA	0xAA806355	AA80FF55
AND	0111	0xA55A00FF	0x5A5AFFFF	005A00FF
	0111	0xC3C3F966	0xFF669F5A	C3429942
OR	0110	0x9A9AC300	0x65A3CC0F	FFBBCF0F
	0110	0xC3C3F966	0xFF669F5A	FFE7FF7E
XOR	0100	0xAA5500FF	0x5AA50FF0	F0F00F0F
	0100	0xA5A56C6C	0xFF00C6FF	5AA5AA93
SRL	0101	0x805A6CF3	0x00000010	0000805A
	0101	0x705A6CF3	0x00000005	0382D367
	0101	0x805A6CF3	0x00000000	805A6CF3
	0101	0x805A6CF3	0x00000100	00000000
SLL	0001	0x805A6CF3	0x00000010	6CF30000
	0001	0x805A6CF3	0x00000005	0B4D9E60
	0001	0x805A6CF3	0x00000100	00000000
SRA	1101	0x805A6CF3	0x00000010	0000805A
	1101	0x705A6CF3	0x00000005	0382D367
	1101	0x805A6CF3	0x00000000	805A6CF3
	1101	0x805A6CF3	0x00000100	00000000
SLT	0010	0x7FFFFFFFF	0x80000000	00000000
	0010	0x80000000	0x00000001	00000001
	0010	0x00000000	0x00000000	00000000
	0010	0x55555555	0x55555555	00000000

SLTU	0011	0x7FFFFFFF	0x80000000	00000001
	0011	0x80000000	0x00000001	00000000
	0011	0x00000000	0x00000000	00000000
	0011	0x55AA55AA	0x55AA55AA	00000000
LUI COPY	1001	0x01234567	0x76543210	01234567
	1001	0xFEDCBA98	0x89ABCDEF	FEDCBA98

Simulation:



5. System Verilog Source Code:

For ALU:

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: Cal Poly SLO
// Engineer: Wyatt Tack
//
// Create Date: 01/24/2024
// Design Name: ALU
// Project Name: OTTER MCU
// Target Devices: Basys 3 Board
// Description: Arithmetic Logic Unit, processes functions
//              on OTTER MCU
//
/////////////////////////////////////////////////////////////////


module ALU(
input  [31:0] ALU_srcA, //Only 2 inputs, a select for the
input  [31:0] ALU_srcB, //operation, and the output
input  [3:0]  ALU_FUN,
output logic [31:0] result
);
always_comb
begin          //combinational multiplexor of logic circuits
case (ALU_FUN) //case statement outputs data to result
4'b0000: result = ALU_srcA + ALU_srcB; //add
4'b1000: result = ALU_srcA - ALU_srcB; //sub
4'b0110: result = ALU_srcA | ALU_srcB; //or
4'b0111: result = ALU_srcA & ALU_srcB; //and
4'b0100: result = ALU_srcA ^ ALU_srcB; //xor
4'b0101: result = ALU_srcA >> ALU_srcB; //SRL
4'b0001: result = ALU_srcA << ALU_srcB; //SLL
4'b1101: result = ALU_srcA >>> ALU_srcB; //SRA
4'b0010: if($signed(ALU_srcA) < $signed(ALU_srcB))
           result = 32'h00000001; //SLT
           else result = 32'h00000000;
4'b0011: if(ALU_srcA < ALU_srcB)
           result = 32'h00000001; //SLTU
           else result = 32'h00000000;
4'b1001: result = ALU_srcA; //LUI-copy
default: result = 32'hafafbcbcb;
endcase
end
endmodule
```

For ALU Simulation Test Bench:


```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: Cal Poly SLO
// Engineer: Wyatt Tack
//
// Create Date: 01/24/2024
// Design Name: ALU Test Bench
// Project Name: OTTER MCU
// Target Devices: Basys 3 Board
// Description: Arithmetic Logic Unit, processes functions
//              on OTTER MCU simulation source
/////////////////////////////////////////////////////////////////
module ALU_TB();
  logic [31:0] ALU_srcA; //same inputs and outputs as ALU,
  logic [31:0] ALU_srcB; //test cases received from CPE 233
  logic [3:0] ALU_FUN;   //lab manual
  logic [31:0] result;
  ALU UUT (.ALU_srcA(ALU_srcA), .ALU_srcB(ALU_srcB), .ALU_FUN(ALU_FUN), .result(result));
  always begin
#10 ALU_FUN = 4'b0000; //add cases
    ALU_srcA = 32'hA50F96C3;
    ALU_srcB = 32'h5AF0693C;
#10 ALU_srcA = 32'h84105F21;
    ALU_srcB = 32'h7B105FDE;
#10 ALU_srcA = 32'hFFFFFFF;
    ALU_srcB = 32'h00000001;
#10 ALU_FUN = 4'b1000; //sub cases
    ALU_srcA = 32'h00000000;
    ALU_srcB = 32'h00000001;
#10 ALU_srcA = 32'hAA806355;
    ALU_srcB = 32'h550162AA;
#10 ALU_srcA = 32'h550162AA;
    ALU_srcB = 32'hAA806355;
#10 ALU_FUN = 4'b0111; //and cases
    ALU_srcA = 32'hA55A00FF;
    ALU_srcB = 32'h5A5AFFFF;
#10 ALU_srcA = 32'hC3C3F966;
    ALU_srcB = 32'hFF669F5A;
#10 ALU_FUN = 4'b0110; //or cases
    ALU_srcA = 32'h9A9AC300;
    ALU_srcB = 32'h65A3CC0F;
#10 ALU_srcA = 32'hC3C3F966;
    ALU_srcB = 32'hFF669F5A;
#10 ALU_FUN = 4'b0100; //xor cases
    ALU_srcA = 32'hAA5500FF;
    ALU_srcB = 32'h5AA50FF0;
#10 ALU_srcA = 32'hA5A56C6C;
    ALU_srcB = 32'hFF00C6FF;
#10 ALU_FUN = 4'b0101; //srl cases
    ALU_srcA = 32'h805A6CF3;
    ALU_srcB = 32'h00000010;
#10 ALU_srcA = 32'h705A6CF3;
    ALU_srcB = 32'h00000005;
#10 ALU_srcA = 32'h805A6CF3;
    ALU_srcB = 32'h805A6CF3;
#10 ALU_srcA = 32'h805A6CF3;
    ALU_srcB = 32'h00000000;
#10 ALU_srcA = 32'h805A6CF3;
    ALU_srcB = 32'h00000100;
#10 ALU_FUN = 4'b0001; //sll cases
    ALU_srcA = 32'h805A6CF3;
    ALU_srcB = 32'h00000010;
#10 ALU_srcA = 32'h805A6CF3;
    ALU_srcB = 32'h00000005;
#10 ALU_srcA = 32'h805A6CF3;
    ALU_srcB = 32'h805A6CF3;
#10 ALU_srcA = 32'h805A6CF3;
    ALU_srcB = 32'h00000000;
#10 ALU_srcA = 32'h805A6CF3;
    ALU_srcB = 32'h805A6CF3;
#10 ALU_FUN = 4'b1101; //sra cases
    ALU_srcA = 32'h805A6CF3;
    ALU_srcB = 32'h00000010;
#10 ALU_srcA = 32'h705A6CF3;
    ALU_srcB = 32'h00000005;
#10 ALU_srcA = 32'h805A6CF3;
    ALU_srcB = 32'h805A6CF3;
#10 ALU_srcA = 32'h805A6CF3;
    ALU_srcB = 32'h00000000;
#10 ALU_srcA = 32'h805A6CF3;
    ALU_srcB = 32'h00000100;
#10 ALU_FUN = 4'b0010; //slt cases
    ALU_srcA = 32'h7FFFFFFF;
    ALU_srcB = 32'h80000000;
#10 ALU_srcA = 32'h80000000;
    ALU_srcB = 32'h80000000;
#10 ALU_srcA = 32'h00000001;
    ALU_srcB = 32'h00000000;
#10 ALU_srcA = 32'h00000000;
    ALU_srcB = 32'h00000000;
#10 ALU_srcA = 32'h55555555;
    ALU_srcB = 32'h55555555;
#10 ALU_FUN = 4'b0011; //sltu cases
    ALU_srcA = 32'h7FFFFFFF;
    ALU_srcB = 32'h80000000;
#10 ALU_srcA = 32'h80000000;
    ALU_srcB = 32'h80000000;
#10 ALU_srcA = 32'h00000001;
    ALU_srcB = 32'h00000000;
#10 ALU_srcA = 32'h00000000;
    ALU_srcB = 32'h00000000;
#10 ALU_srcA = 32'h55AA55AA;
    ALU_srcB = 32'h55AA55AA;
#10 ALU_FUN = 4'b1001; //lui-copy cases
    ALU_srcA = 32'h01234567;
    ALU_srcB = 32'h76543210;
#10 ALU_srcA = 32'hEDCBA98;
    ALU_srcB = 32'h89ABCDEF;
  end
endmodule
```

Part 2:

 1. Behavior Description: The immediate generator (IMMED_GEN) is used to take in the machine code, and for each type of code that the machine code could produce an immediate for it. There are 5 different types of immediate, so the Immediate generator produces them all in parallel, and through the other parts of the machine code help select which of those immediate are actually meant to be used. Each different type of machine code lays out the immediate values differently in its set of binary instruction values, so concatenation is used in the IMMED_GEN to untangle the bits into the organized way they should be.
2. Structural Design:



3. Synthesis Warnings Listing:

 

4. Verification:
 - a. Assembly code used to create machine code with immediates:

```
lui x6, 0x1a           #U-Type
addi x6, x7, 0x2b       #I-Type
sw x6, 0x3c(x7)         #S-Type
jal x6, EIGHT           #J-Type
beq x6, x7, TWELVE      #B-Type

EIGHT:
nop
nop #last sets of nop used to
TWELVE:
nop #set labels for j and b
```

b. Test Case Table:

Test Case Input	Test Case Output	Test Case Reasoning
0001a337 lui x6, 0x1a	U-Type = 0001a000	Tests U-Type command LUI
02b38313 addi x6, x7, 0x2b	I-Type = 0000002b	Tests I-Type command ADDI
0263ae23 sw x6, 0x3c(x7)	S-Type = 0000003c	Tests S-Type command SW
0080036f jal x6, EIGHT	J-Type = 00000008	Tests J-Type command JAL
00730663 beq x6, x7, TWELVE	B-Type = 0000000c	Tests B-Type command BEQ

c. Simulation:

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns	40.000 ns	50.000 ns
> Instruction[31:0]	0001a337	XXXXXXXX	0001a337	02b38313	0263ae23	0080036f	00730663
> U_Type[31:0]	0001a000	XXXXX000	0001a000	02b38000	0263a000	00800000	00730000
> I_Type[31:0]	00000000	XXXXXXXX	00000000	0000002b	00000026	00000008	00000007
> S_Type[31:0]	00000006	XXXXXXXX	00000006	00000026	0000003c	00000006	0000000c
> J_Type[31:0]	0001a000	XXXXXXXX	0001a000	0003882a	0003a026	00000008	00030806
> B_Type[31:0]	00000006	XXXXXXXX	00000006	00000026	0000003c	00000006	0000000c

5. System Verilog Source Code:

a. IMMED_GEN:

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: Cal Poly SLO
// Engineer: Wyatt Tack
//
// Create Date: 01/24/2024
// Design Name: IMMED_GEN
// Project Name: OTTER MCU
// Target Devices: Basys 3 Board
// Description: Generates Immediate numbers needed from
//              different instruction types in assembly
//
/////////////////////////////////////////////////////////////////
module IMMED_GEN(
input  [31:0] Instruction, //full machine code
output [31:0] U_Type, I_Type, S_Type, J_Type, B_Type
); //5 assignments of concatenation for different types
assign U_Type = {Instruction[31:12], {12{1'b0}}};
assign I_Type = {{20{Instruction[31]}}, Instruction[30:20]};
assign S_Type = {{20{Instruction[31]}}, Instruction[30:25],
                 Instruction[11:7]};
assign J_Type = {{11{Instruction[31]}}, Instruction[19:12],
                 Instruction[20],
                 Instruction[30:21], 1'b0};
assign B_Type = {{19{Instruction[31]}}, Instruction[7],
                 Instruction[30:25],
                 Instruction[11:8], 1'b0};
endmodule
```


b. IMMED_GEN Simulation Source:

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: Cal Poly SLO
// Engineer: Wyatt Tack
//
// Create Date: 01/24/2024
// Design Name: IMMED_GEN_TB
// Project Name: OTTER MCU
// Target Devices: Basys 3 Board
// Description: Generates Immediate numbers needed from
//              different instruction types in assembly
//              Simulation Source
/////////////////////////////////////////////////////////////////
module IMMED_GEN_TB();
  logic [31:0] Instruction; //full machine code
  logic [31:0] U_Type, I_Type, S_Type, J_Type, B_Type;
  IMMED_GEN UUT (Instruction, .U_Type(U_Type),
                 .I_Type(I_Type), .S_Type(S_Type),
                 .J_Type(J_Type), .B_Type(B_Type));

  always begin
    #10 Instruction = 32'h0001a337; //copied machine code from
    #10 Instruction = 32'h02b38313; //RARS and the assembly
    #10 Instruction = 32'h0263ae23; //code
    #10 Instruction = 32'h0080036f;
    #10 Instruction = 32'h00730663;

  end
endmodule
```